

EXERCISES

AC CIRCUITS [Even numbers]

1. Explain why in a circuit containing L and C, current is maximum or minimum at a particular frequency. A series tuned circuit is to be resonant at 800 kHz. If $L = 40$ microHenry with $R = 4.02$ ohms, determine the value of C required. (0.99 nF, 16 kHz)

2. A 200 microHenry coil in series with a capacitor form a circuit resonant at 800 kHz. When the circuit is connected across a constant voltage of 800 kHz frequency, the voltage across the capacitor is 100 mV. When a non-inductive resistance is connected in series with the tuned circuit, the capacitor voltage fell to 50 mV. Calculate (195 μ F, 50 Ω)

(a) The capacitance

(b) The original series resistance.

3. Derive an expression for the frequency of resonance of the circuit shown in fig.P.2.1 in terms of L and C (40.0 Ω ; 5.0 A; 333 μ F)

(a) Calculate this frequency.

(b) At resonance, determine

(i) The total impedance of the circuit

(ii) The circuit current

(iii) The value of C to give series resonance with the same coil at

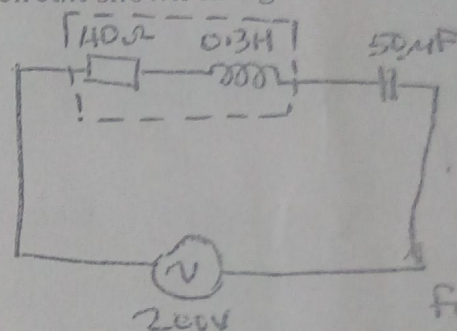


Fig P.2.1

4. A series circuit takes a current of 5 amps at a power factor of 0.866 leading when connected across a 240 volts alternating supply. Draw a simple diagram of the circuit, and calculate (48.0 Ω ; 41.6 Ω ; 24 Ω ; 1039 W; 600 W)

(a) The impedance

(b) The resistance

(c) The reactance

(d) The active power

(e) The reactive power

Sketch the vector diagram.

5. For the circuit of fig.P.2.2, calculate (74.3 Ω ; 10.24 Ω ; 4.26 Ω ; 46.95 A; 4.0 Ω ; 50.0 A) (43.5 W; 43.5 W)

(a) The resistance of the coil

(b) The impedance of the coil

(c) The impedance of the circuit

(d) The circuit current


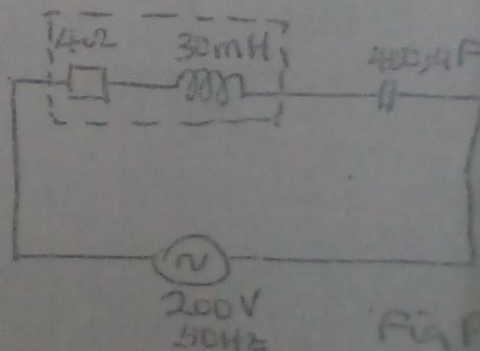


Fig P.2.2

calculate

(a) The impedance and current of the circuit

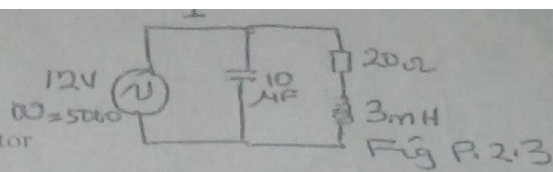(b) The voltage across the coil and the capacitor



6. For the circuit of fig P.2.3, determine the impedances of the two sectors and thence determine the circuit current. $[20.0 \Omega, 25.0 \Omega, 24.3 \Omega, 0.49 A]$

7. A $10 nF$ capacitor is connected in series with a coil of $10 mH$ inductance and a 40Ω resistance. Calculate frequency of resonance. If a voltage of 2 volts is to appear across the capacitor at resonance, what total voltage must be applied to the series combination? $[15.92 kHz, 82.0 mV]$

8. A coil of inductance $0.04 H$ and negligible resistance is connected in parallel with a 10Ω resistor across a 240 volt supply of frequency $50 Hz$. Sketch the vector diagram of the circuit and calculate $[24.0 A, 19.0 A, 43.0 A, 5.76 kW, 0.56]$

(a) The current through the resistor

(b) The current through the coil

(c) The supply current

(d) The power in the circuit

(e) The power factor of the circuit

9. A voltage of 240 volts at a frequency of $50 Hz$ is applied to a circuit which has a 60Ω resistor in parallel with a capacitance of $40 \mu F$. Sketch the phasor or vector diagram for the circuit. Calculate $[4.0 A, 3.0 A, 7.0 A, 0.57, 960 W]$

(a) The resistor current

(b) The capacitor current

(c) The supply current

(d) The power factor

(e) The active power

10. A coil of $L=10 mH$ and $R=5 \Omega$ is connected in series with a $0.0002 \mu F$ capacitor, and a voltage of $1 mV$ (rms) is connected across both components. Calculate $[12.6 kHz, 0.20 A, 1.4]$

(a) The resonance frequency

(b) The current at this frequency

(c) The capacitor voltage at resonance

(d) The power absorbed at resonance

11. A certain coil drew a current of 4 amps (rms) when connected across 240 volts (rms) $50 Hz$ supply. The true power consumed by the coil was found to be 960 watts. Determine the power factor of the coil as well as its resistance. $[0.80, 38.4 \Omega]$


DC CIRCUITS & NETWORK THEOREM

EXERCISES.





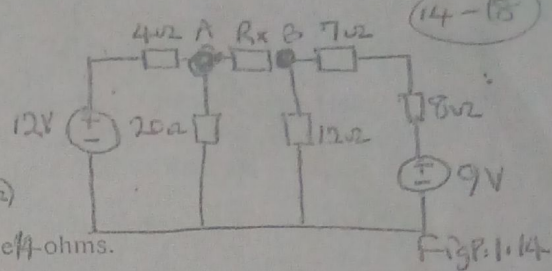
1. State Kirchhoff's laws for networks. Use the appropriate Kirchhoff's law to determine the value of current flowing through the 1 ohm (load) resistance in fig p.1.1 ($0.2625A$)
2. In circuit of fig.p.1.2, calculate the current through the 4 ohms resistance, and the power dissipated in the 12 ohms resistance. ($1.0A$; $6.75W$)
3. In fig p.1.3 circuit, determine the voltage across the 4 ohms resistance, using Kirchhoff's law. ($8.0V$)
4. State Kirchhoff's law. Use this law to determine the current in the 1.6 ohms resistance, and also the voltage across it in p.1.4 ($3.2V$)
5. State the superposition theorem. Use this theorem to determine the current flowing in the 1 ohm resistance of fig.p.1.5 ($0.059A$)
6. In the circuit of fig.p.1.6, determine the value of current flowing through the 8 ohms resistance as well as its direction. ($1.0A \rightarrow$)
7. Fig.1.7 shows a circuit of two voltage sources feeding T-network. Calculate the value of the current marked A, B, C. [$0.5A$; $1.67A$; $1.17A$]
8. State thevenin's network theorem. For the circuit of fig.p.1.8, calculate ($1.67A$; $0.14W$)
 - (a) The current along the arm XY
 - (b) The power dissipated in the 3.5 ohms resistance.
9. Use the superposition theorem to determine ($1.14A$; $4.0W$)
 - (a) The current supplied by the 6-volts battery,
 - (b) The power dissipated by the battery in fig.p.1.9
10. Use Kirchhoff's voltage law to determine the source current as well as the current flowing in the 20 ohms resistance of fig.1.10 ($7.0A$; $1.0A$)
11. Determine the equivalent Thevenin (circuit) diagram of fig.1.11, clearly giving the value of the equivalent voltage and resistance. ($5.0V$; 17.5Ω)
12. In fig.1.12, determine the current flowing through the 10 ohms resistance. Determine also the voltage developed across the 4 ohms resistance. ($3.0A$; $12.0V$)
13. Fig.p.1.13 shows a bridge...T circuit. Determine the voltages across the resistance of 5 ohms and 2 ohms ($3.0V$; $8.0V$)

For the circuit of fig.P.1.14, calculate with to terminals AB

- The Thevenin equivalent voltage and resistance, $(6.0V, 10\Omega)$
- The value of R_x to dissipate maximum energy, (10Ω)
- The current in and the voltage across R_x if its value is 4Ω -ohms. $(0.25A, 3.5V)$



- State norton's network theorem. Determine the Norton equivalent circuit parameters to the circuit of fig.p.1.15. $(1.75A, 6.4\Omega)$
- You are given the circuit of fig.P.1.16, calculate the current in the 10 ohms resistance. $(4.53A)$
- Find the Thevenin equivalent of fig.P.1.17 circuit $(1.2V, 75.0\Omega)$
- Explain why kirchhoff's current law is regarded as a statement of conservation of electric charge. Use this law to determine the current flowing through resistor R_6 in fig.P.1.18. You are given that $E=2$ volts, $R_1=500$ ohms, $R_2=1000$ ohms, $R_3=400$ ohms, $R_4=800$ ohms, $R_5=500$ ohms, $R_6=400$ ohms $(113.0\mu A)$
- If all the resistance in fig.P.1.18 have their values halved when $E=4$ volts, determine the current in R_6 $(3.07mA)$
- Still using fig.P.1.18, determine the value of the current from the battery when the component retain their values as in question 19. $(5.73mA)$
- Deduce the Theveninequivalentcircuit for terminals AB in fig,P,1.19.State the value of the impedance which will be connected across AB to give maximum power output. Calculate this maximum power. $[Take V_{th}=15V] [300+j300\Omega; 300-j300\Omega; 0.24W]$

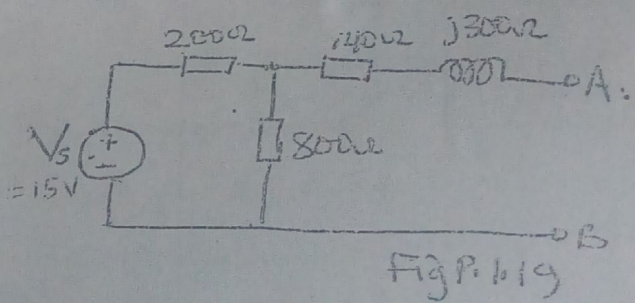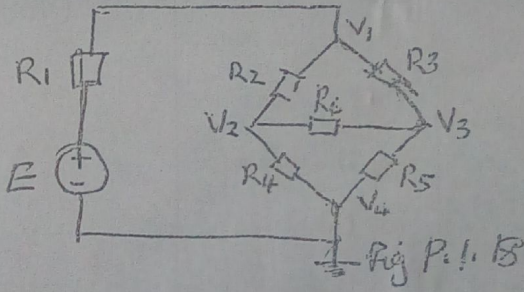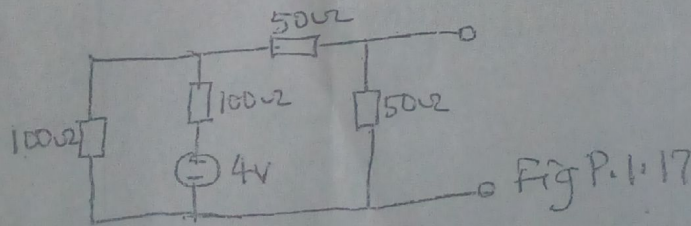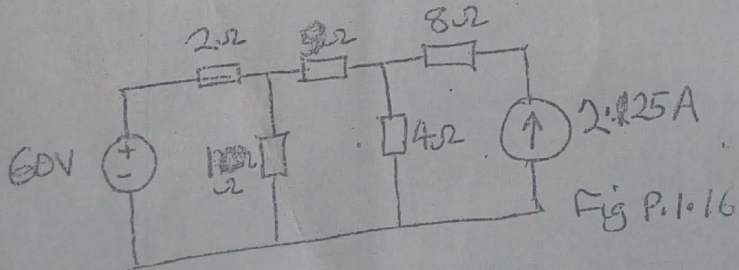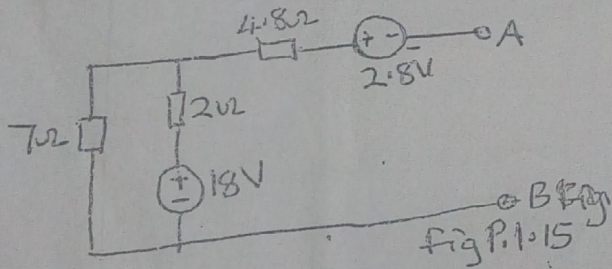

(3)